

非接觸式馬達驅動與伺服控制關鍵技術之開發  
**Study of Key Technologies for Motor Driver and Servo  
Control Using a Contactless Power System**

---

Department of Electrical Engineering  
National Changhua University of Education

Ying-Shing Shiao

2011/01/25

1

**Outline**

---


- Introduction**
- Motivation**
- System Configuration**
- Simulation and Experimental Results**
- Conclusions**

2011/01/25

2
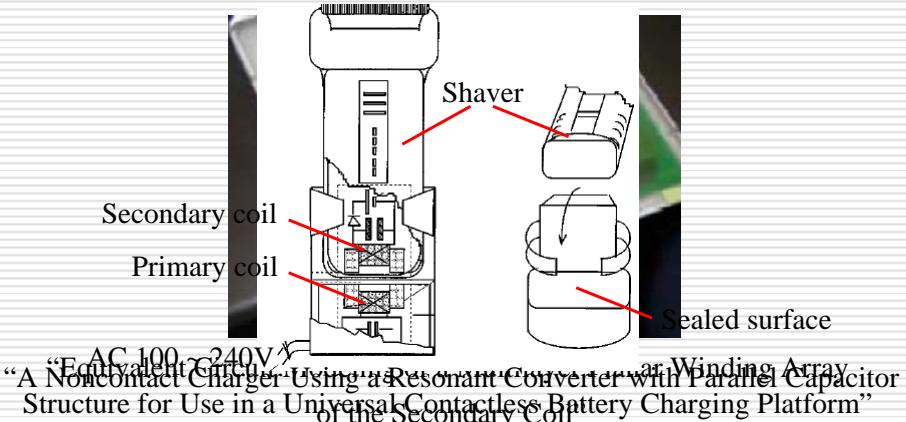
## Introduction

- low power applications for portable electronic devices




2011/01/25

3
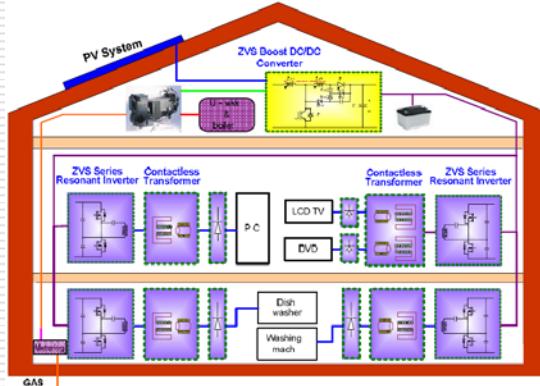
## Introduction

- middle power applications for home electric systems




"A Contactless Power Supply for Photovoltaic Power Generation System"

2011/01/25

4
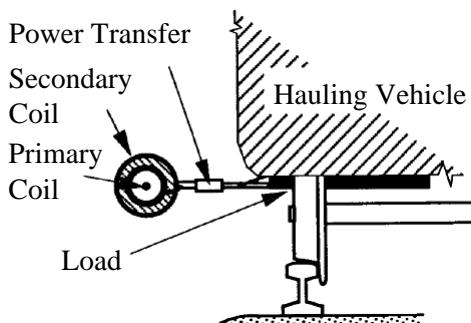
## Introduction

- high power applications for public transport systems



“Contactless Power Delivery System for Mining Applications”


2011/01/25

5


## Motivation




Electric vehicle

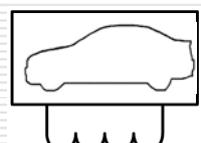


Electric vehicle

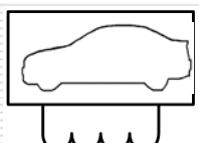

Electric vehicle


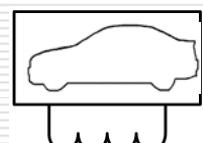


Pickup L<sub>s</sub>

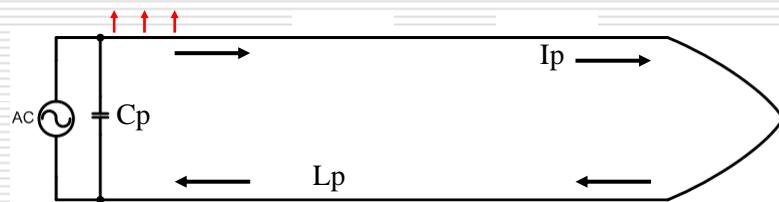


2011/01/25 Primary track / coil inductance is buried in the ground

6

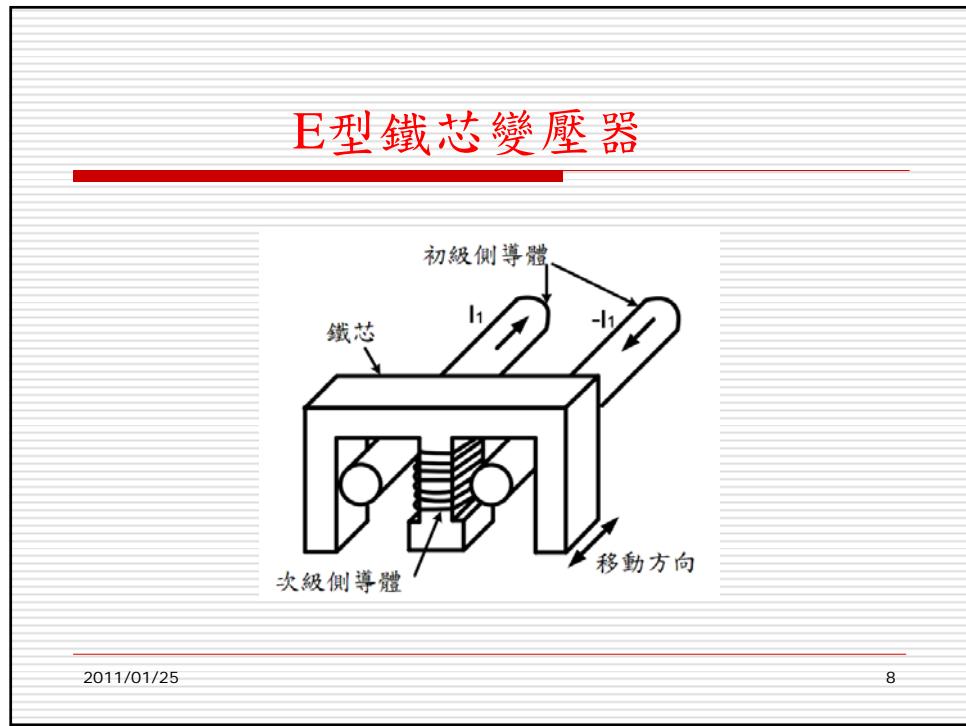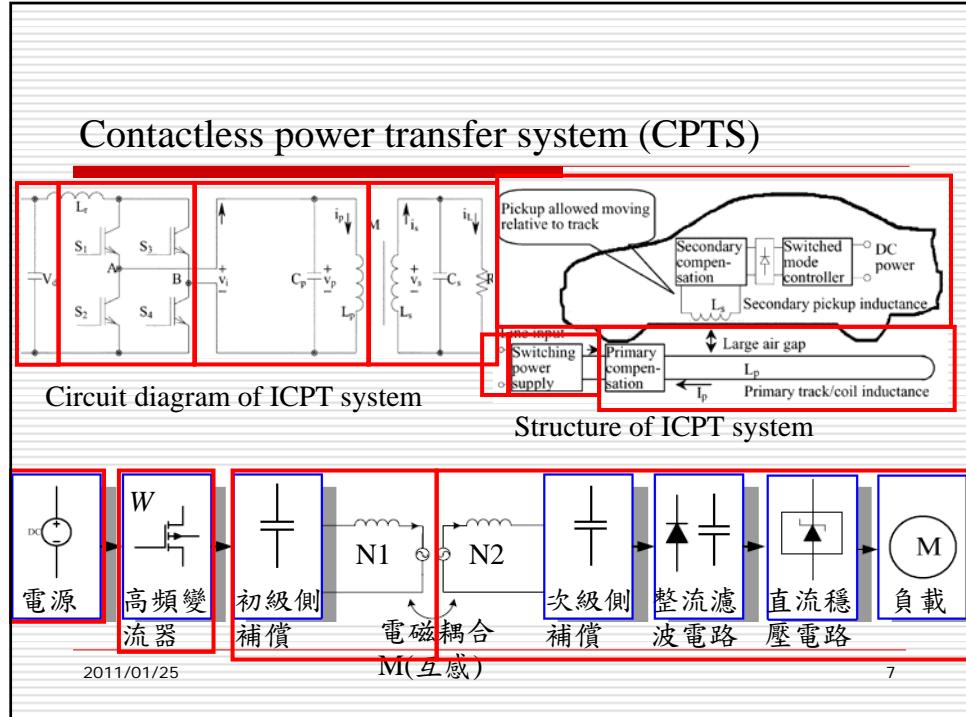


## ECT的磁通分佈

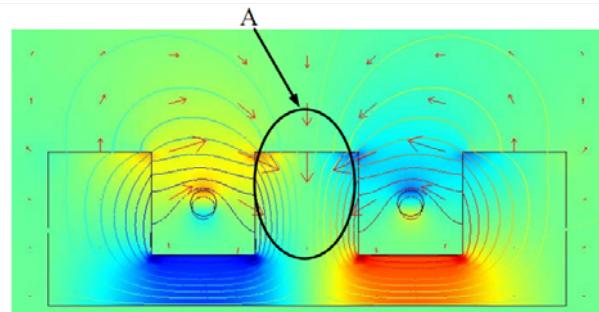

2011/01/25

9


## 非接觸式U型鐵芯應用於運輸系統

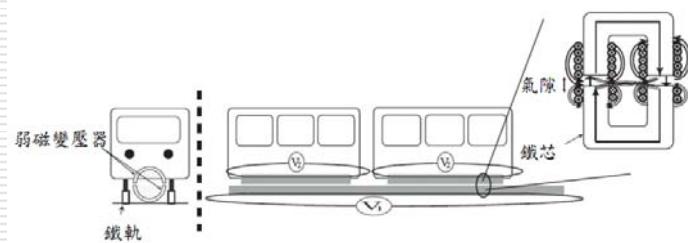

2011/01/25


10

## U型或C型鐵芯變壓器

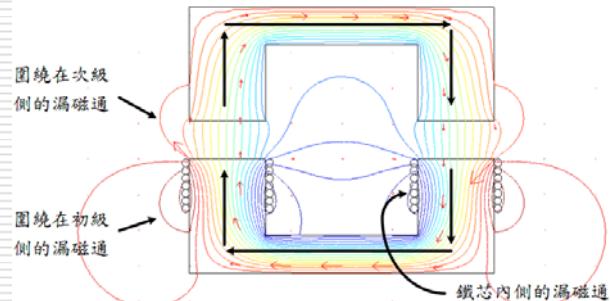

2011/01/25


11

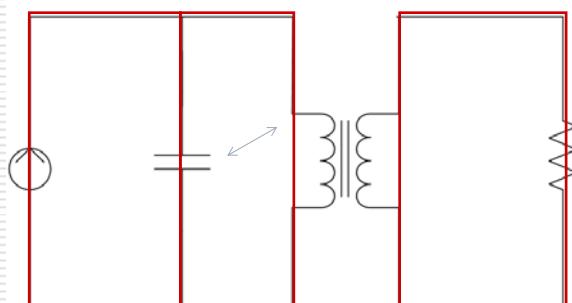

2011/01/25

12


## An LCL load resonant inverter

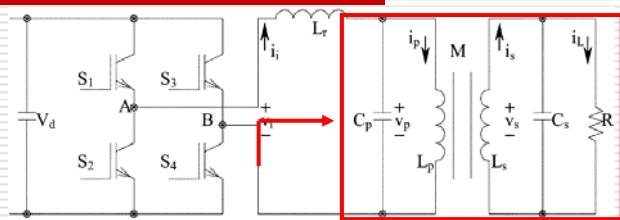

2011/01/25

13


## An LCL load resonant inverter

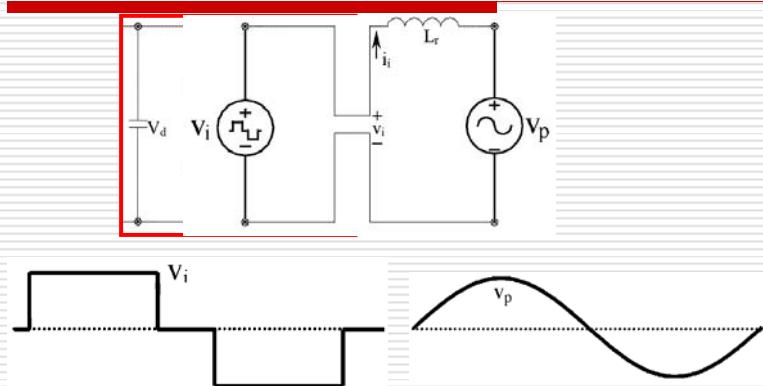

2011/01/25

14


## An LCL load resonant inverter

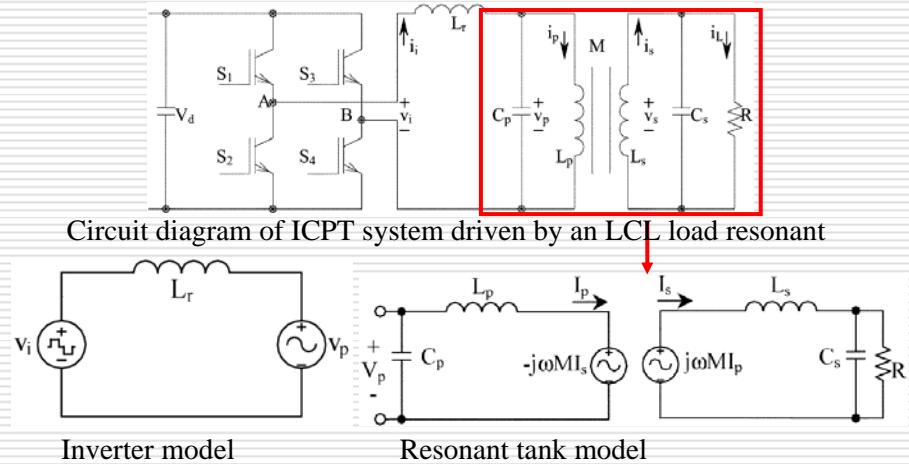

2011/01/25

15



## Inverter model

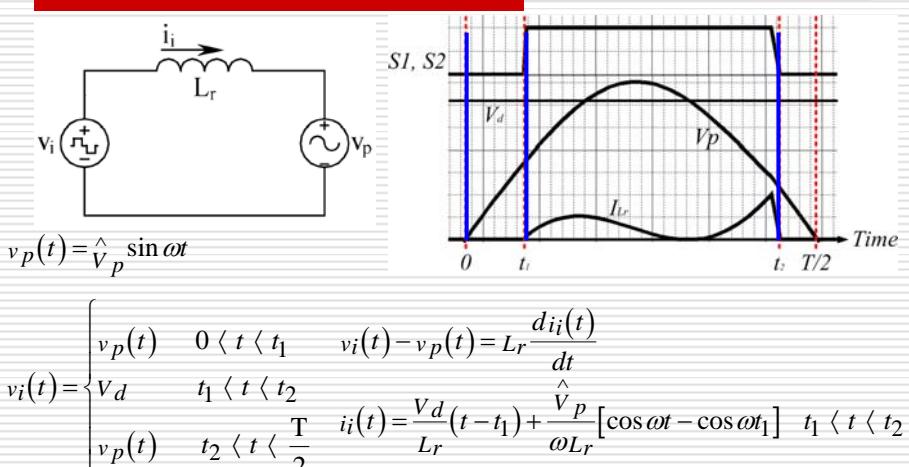

2011/01/25

16

## Inverter model

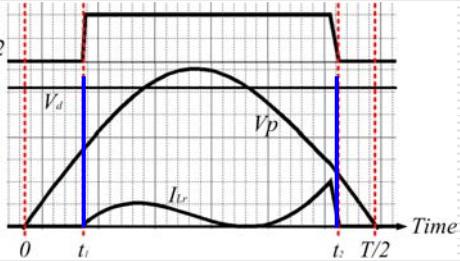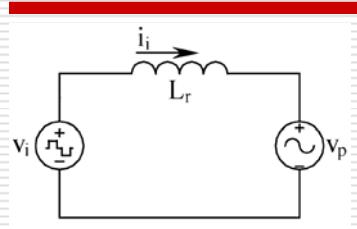

$$P_i = \frac{2V_d}{T} \int_0^T i_i(t) dt$$



$$i_i(t) = \frac{V_d}{L_r} (t - t_1) + \frac{\hat{V}_p}{\omega L_r} [\cos \omega t - \cos \omega t_1] \quad t_1 < t < t_2$$

$$P_i = \frac{\omega V_d^2}{2\pi L_r} (t_2 - t_1)^2 + \frac{V_d \hat{V}_p}{\pi \omega L_r} (\sin \omega t_2 - \sin \omega t_1 - \omega (t_2 - t_1) \cos \omega t_1)$$

2011/01/25

17


## Timing sequence and waveform diagrams

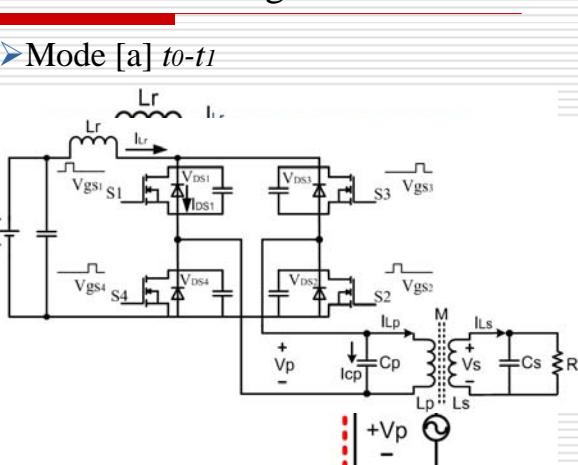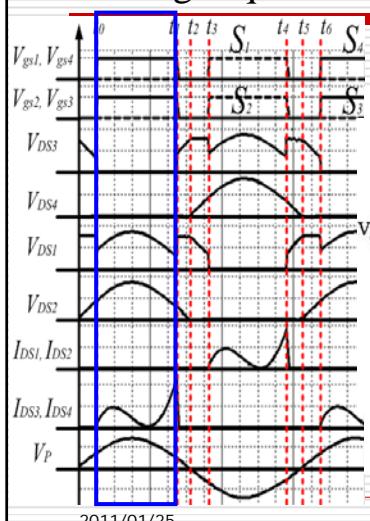


2011/01/25

18

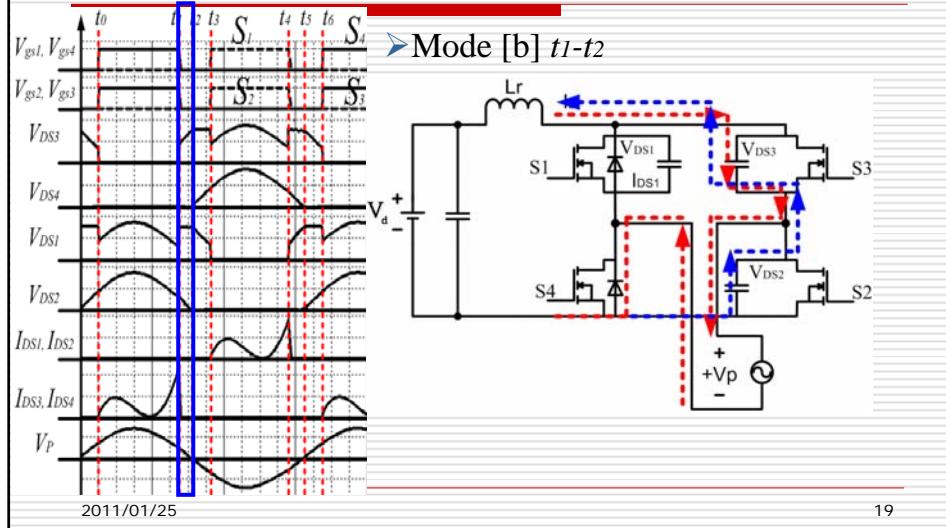
### Timing sequence and waveform diagrams



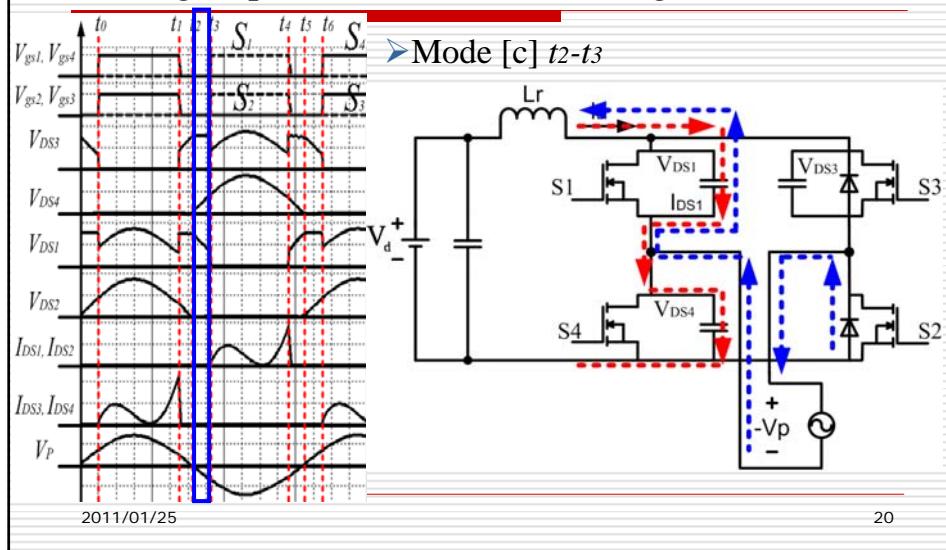
### Timing sequence and waveform diagrams



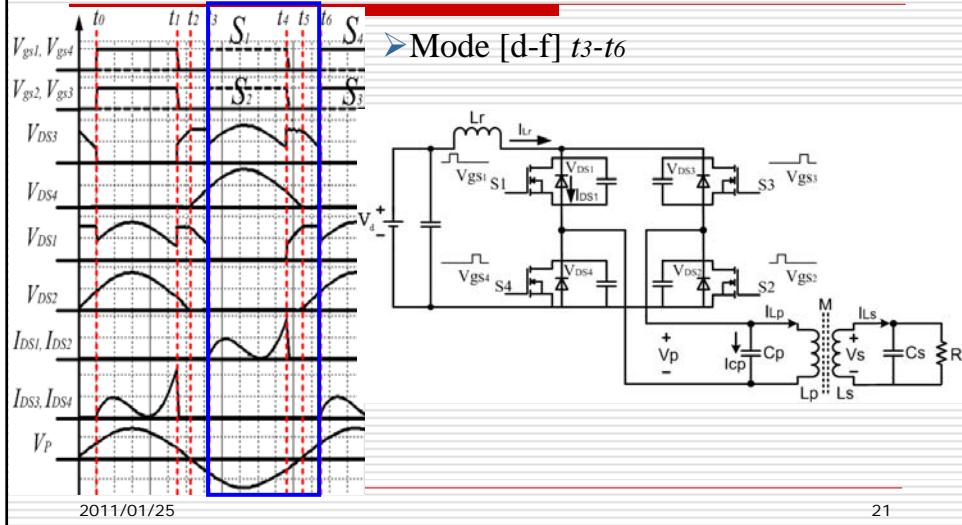
### Timing sequence and waveform diagrams



### Resonant tank model

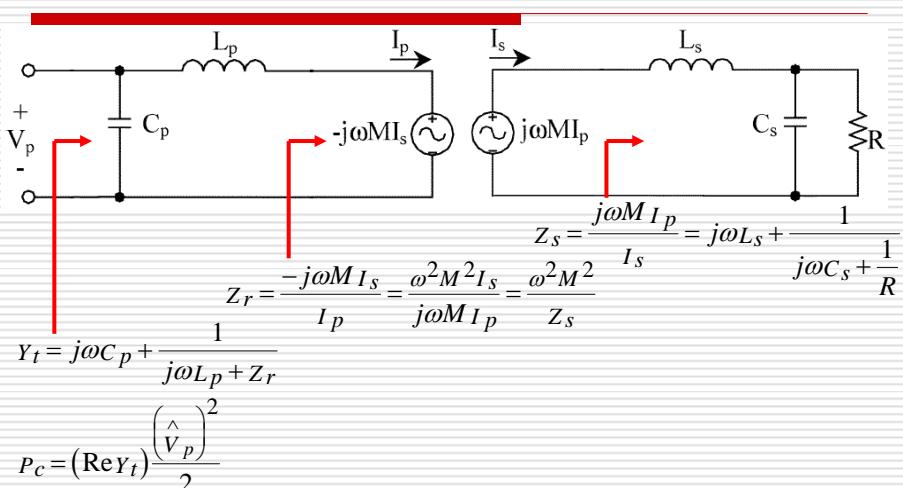

## Resonant tank model

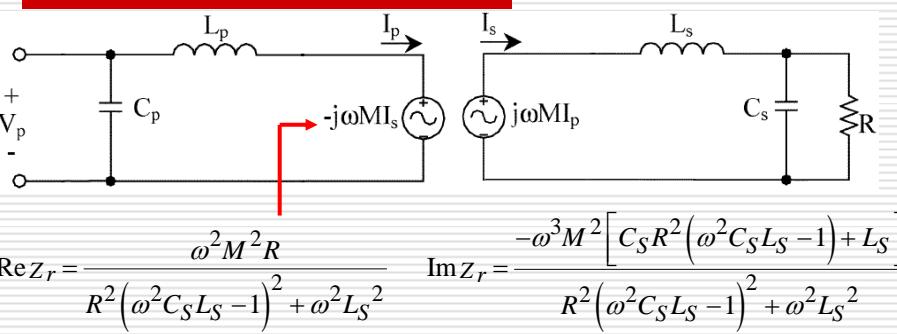


➤ Parameters of the resonant tank circuit :

$$L_P = 19.56 \mu H, L_S = 21.29 \mu H, M = 4.861 \mu H, C_P = 5 \mu F, \text{ and } C_S = 4.648 \mu F$$

2011/01/25

23


## Resonant tank model

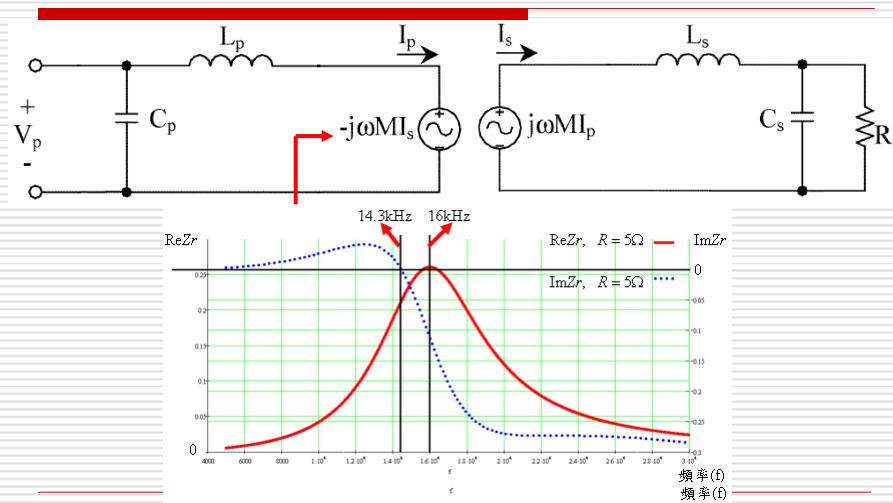

2011/01/25

24

## Resonant tank model

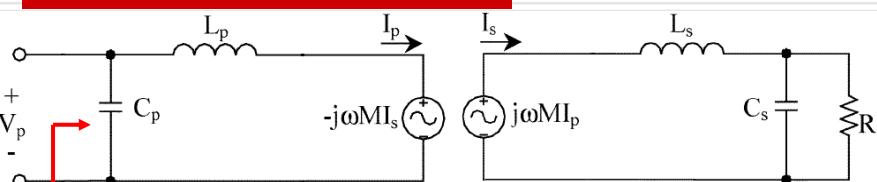


$$\text{Re } Y_n = \frac{\text{Re } Z_r}{\text{Re } Z_{r0}} \left( \frac{\text{Re } Z_r}{\text{Re } Z_{r0}} \right)^2 + \left( \frac{\omega L_P}{\text{Re } Z_{r0}} + \frac{\text{Im } Z_r}{\text{Re } Z_{r0}} \right)^2$$

$$\text{Im } Y_n = \omega C_P (\text{Re } Z_{r0}) - \frac{\frac{\omega L_P}{\text{Re } Z_{r0}} + \frac{\text{Im } Z_r}{\text{Re } Z_{r0}}}{\left( \frac{\text{Re } Z_r}{\text{Re } Z_{r0}} \right)^2 + \left( \frac{\omega L_P}{\text{Re } Z_{r0}} + \frac{\text{Im } Z_r}{\text{Re } Z_{r0}} \right)^2}$$

2011/01/25

25

## Resonant tank model

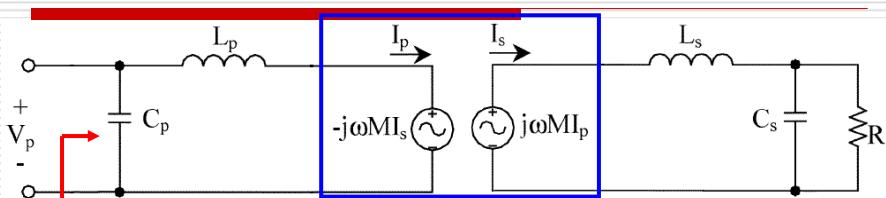


2011/01/25


26

## Inductive transformer

➤Tightly coupled  $k \approx 1$

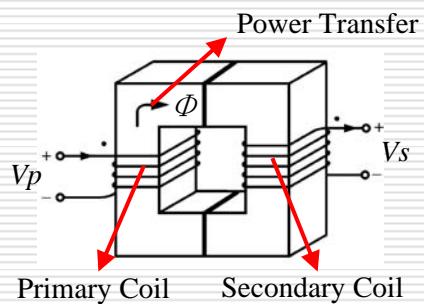


➤Loosely coupled  $k \leq 0.8$

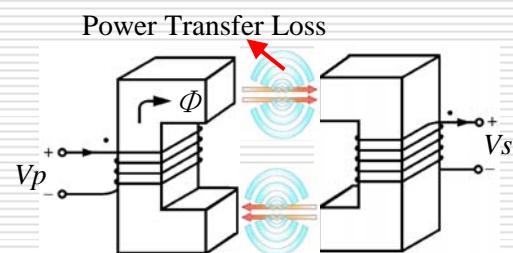

2011/01/25

27


## Proposed LCIT (2-1)

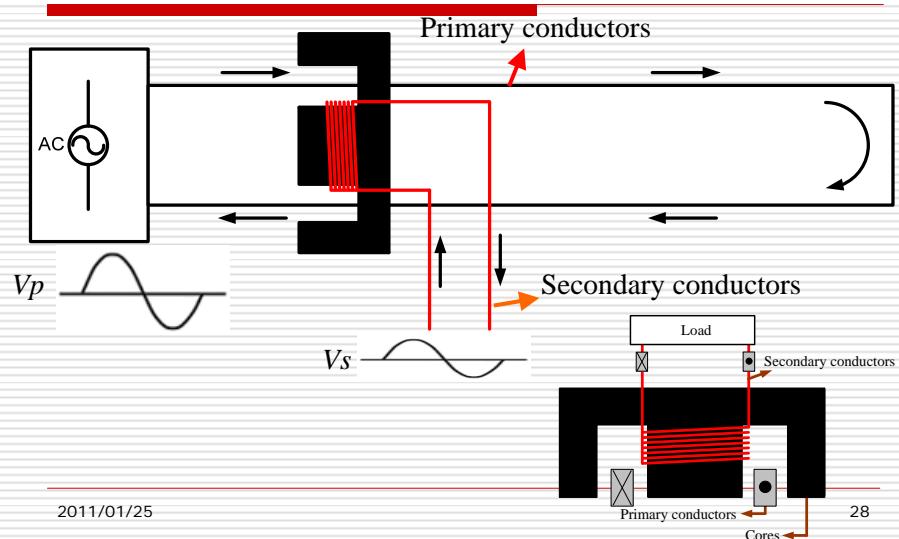

2011/01/25

28


## Proposed LCIT (2-2) $k \leq 0.5$

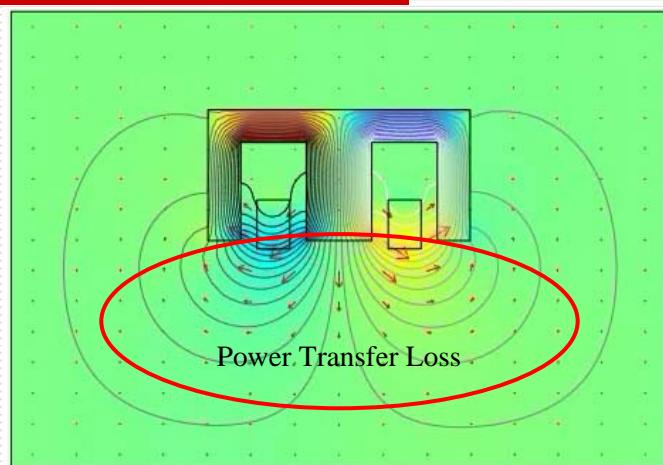

2011/01/25

29


## Prototype power pickup transformer

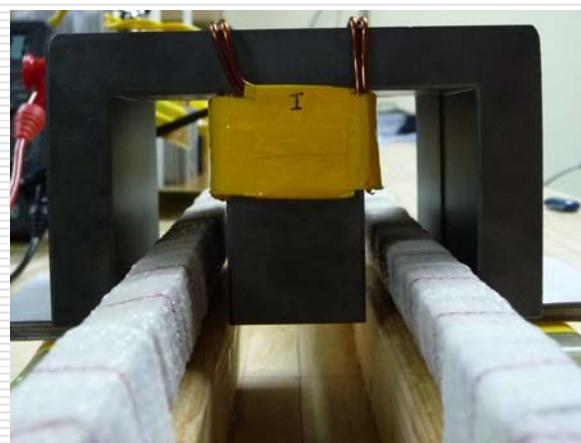

2011/01/25

30

## ControlSystem

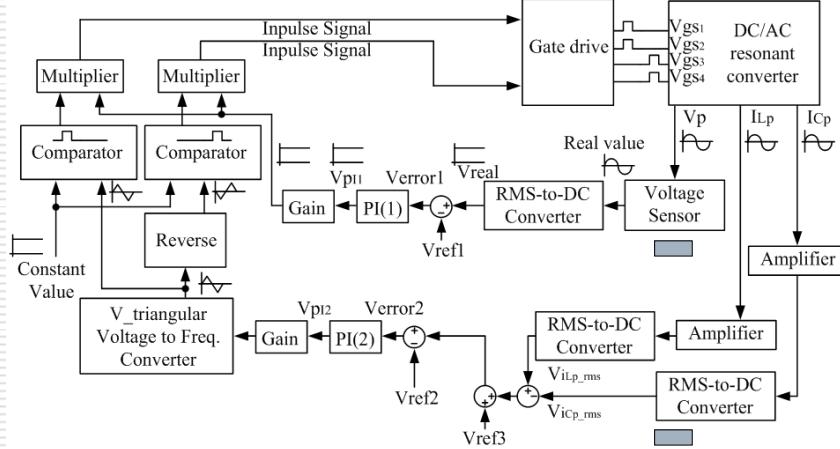

2011/01/25

31


## Parameters of the contactless power transfer system

Nominal frequency	16kHz(15k~17kHz)
Rated power	200VA
Rated load	5Ω
Primary inductance	19.56uH
Primary capacitance	5uF
Mutual inductance	4.861uH
Secondary inductance	21.29uH
Secondary capacitance	1.53uF
Magnetic coupling coefficient	0.238
Np	4
Ns	7
Air gap	20mm


2011/01/25

32

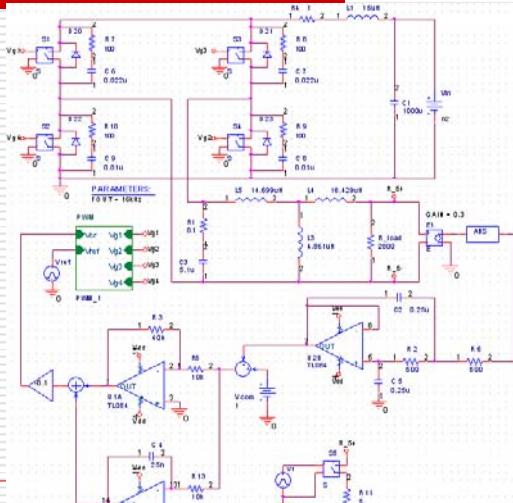
## The simulation configuration of the proposed CPTS



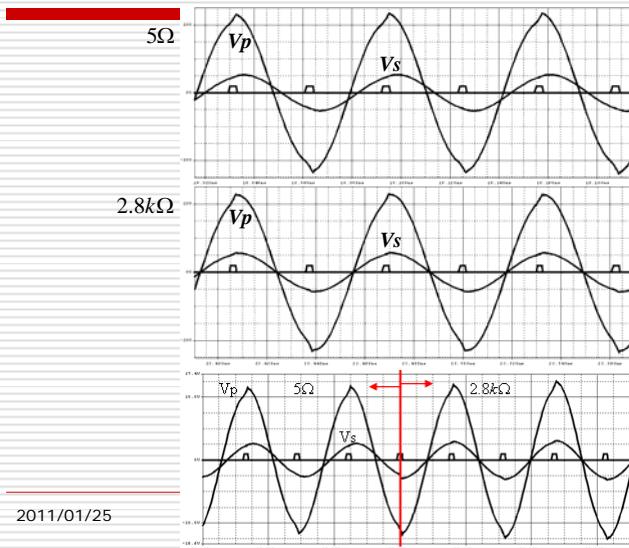
## Simulation result – gate signal, primary and secondary side voltage ( $V_p$ , $V_s$ )



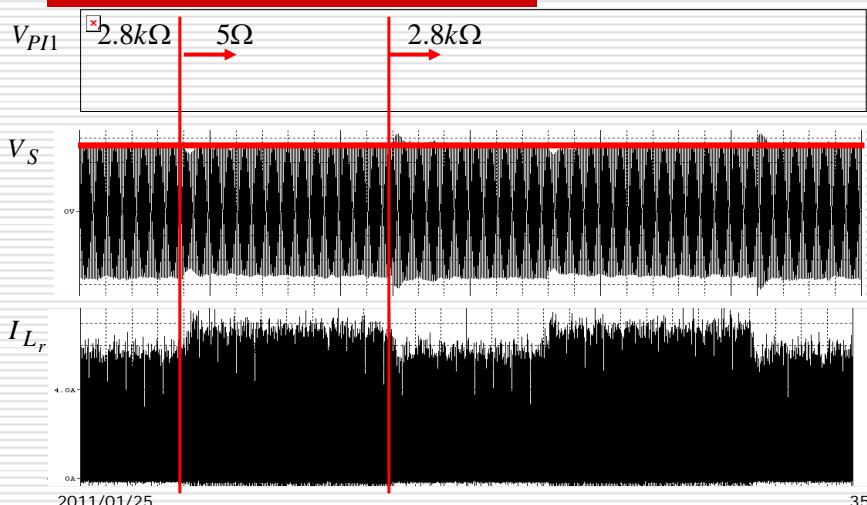
## Simulation result –the transient responses



## Photograph of a primary circuit

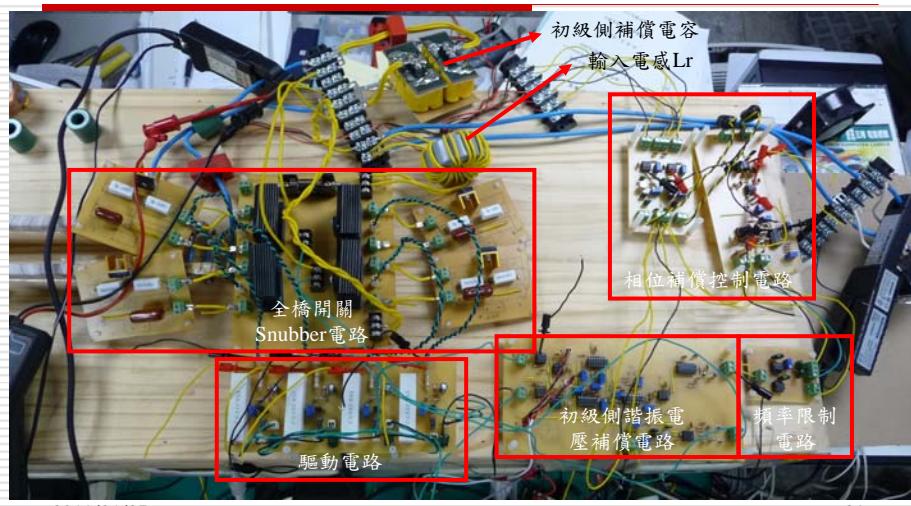


Photograph of two secondary network

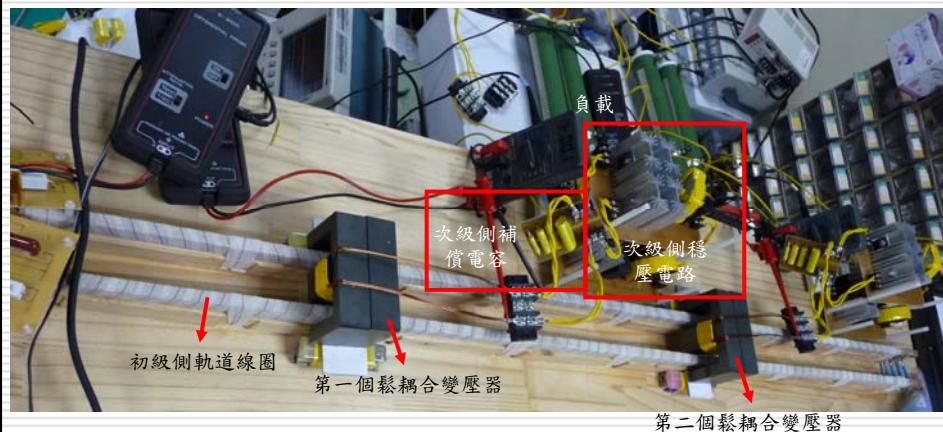

2011/01/25

37

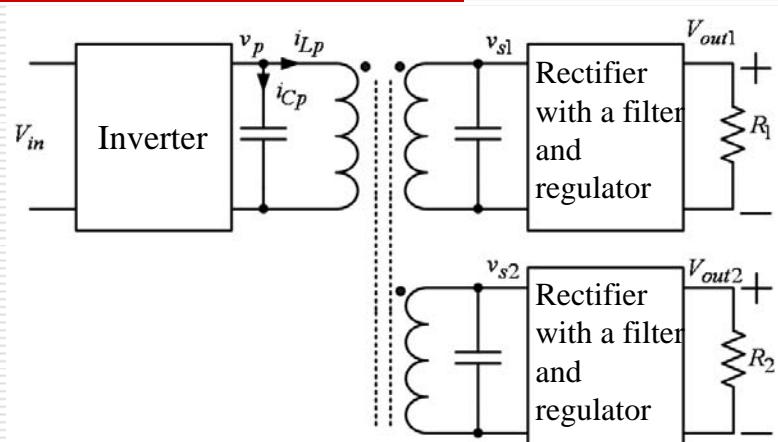
Experimental results –with regulator (SEPIC)



2011/01/25


38
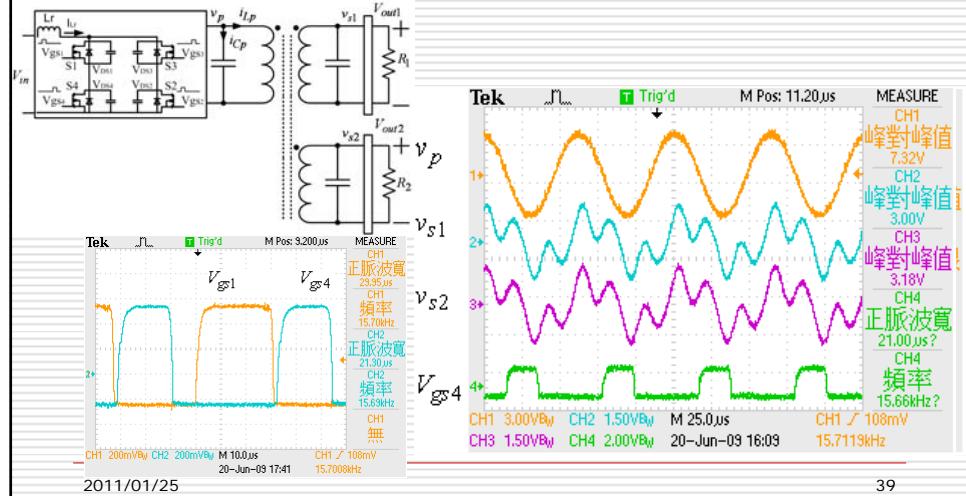
## Experimental results –with regulator (SEPIC)




## With regulator (SEPIC)

Load	$R_1 = 8.3\Omega$ $R_2 = 8.3\Omega$	$R_1 = 8.3\Omega$ $R_2 = 14.2\Omega$	$R_1 = 14.2\Omega$ $R_2 = 14.2\Omega$	$R_1 = 50\Omega$ $R_2 = 14.2\Omega$	$R_1 = 50\Omega$ $R_2 = 50\Omega$
Input power	170.8	141.52	111.63	90.89	70.76
Output power	$P_1 = 36.47$ $P_2 = 36.47$	$P_1 = 36.47$ $P_2 = 21.32$	$P_1 = 21.32$ $P_2 = 21.32$	$P_1 = 6.06$ $P_2 = 21.32$	$P_1 = 6.06$ $P_2 = 6.06$
Efficiency(%)	42.71	40.84	38.2	30.12	17.11

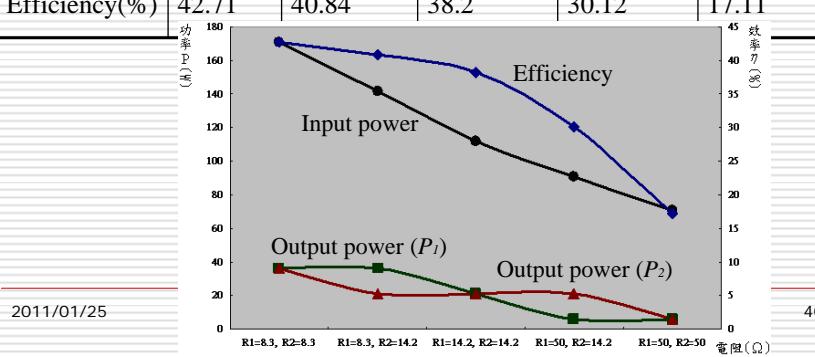

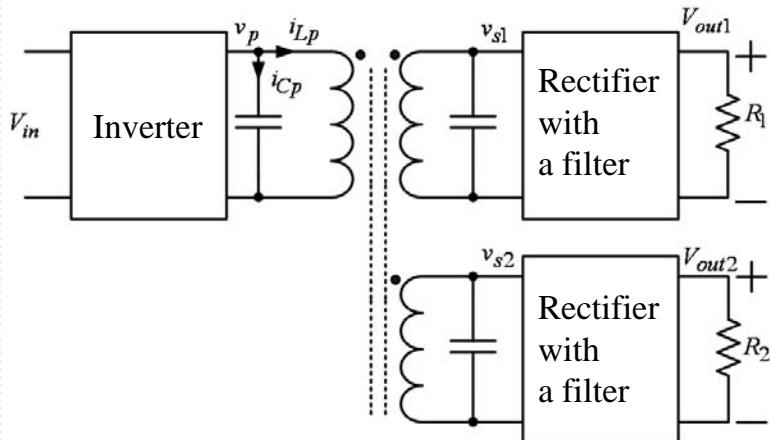
## Experimental results –without regulator



2011/01/25

41
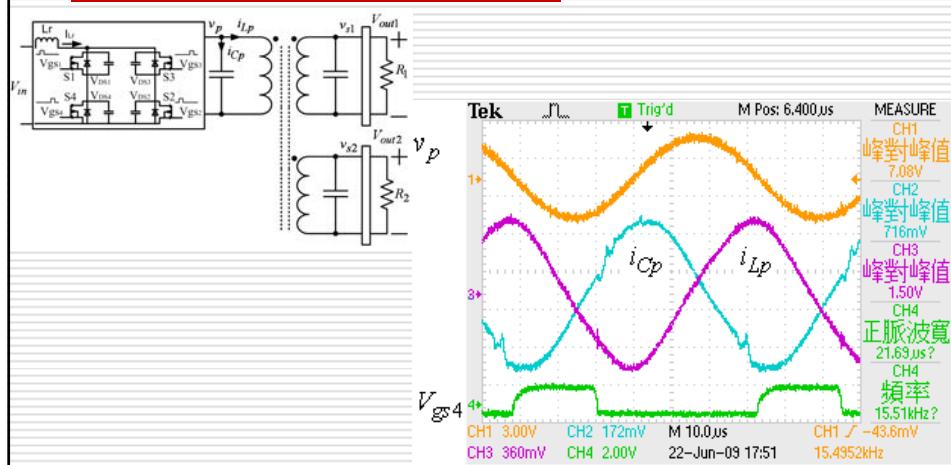
## Experimental results –without regulator




2011/01/25

42

## Without regulator


Load	$R_1 = 4.76\Omega$ $R_2 = 4.76\Omega$	$R_1 = 4.76\Omega$ $R_2 = 9.09\Omega$	$R_1 = 9.09\Omega$ $R_2 = 9.09\Omega$	$R_1 = 100\Omega$ $R_2 = 9.09\Omega$	$R_1 = 100\Omega$ $R_2 = 100\Omega$
Input power	193.37	180.56	167.14	112.85	73.81
Output power	$P_1 = 50.47$ $P_2 = 50.47$	$P_1 = 51.13$ $P_2 = 43.13$	$P_1 = 43.13$ $P_2 = 43.13$	$P_1 = 5.71$ $P_2 = 40.98$	$P_1 = 5.43$ $P_2 = 5.52$
Efficiency(%)	52.2	52.2	51.6	41.37	14.83

2011/01/25

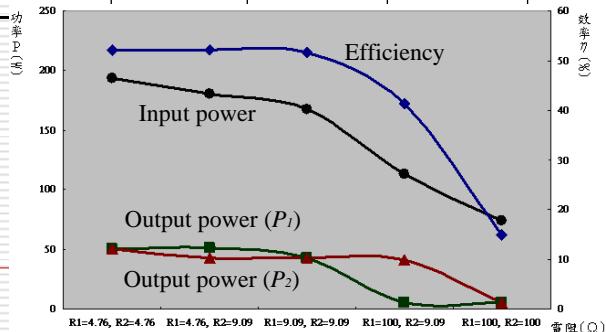


## Converter efficiency

### SEPIC(1)

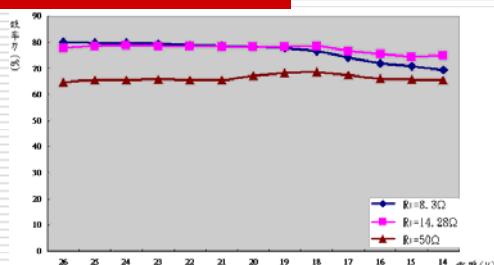

### SEPIC(2)

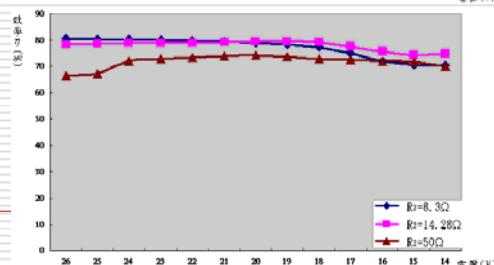

2011/01/25

44

## Conclusions


- Tracking the resonant frequency of coils connected with capacitors can improve the transmission efficiency.
- The system resonant voltage is regulated by a controller when the voltage is changed by the load.
- The overall efficiency is 42.71% in the case of the output current is 4.2A, output voltage is 17.4V, and air gap is 20mm, respectively.

2011/01/25

45

## In further study

### ➤ Microcontroller

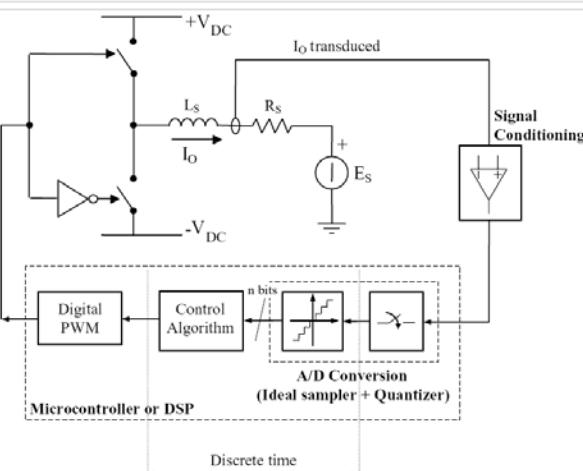

2011/01/25

46

## In further study

### ➤ Different pickup




2011/01/25

47

## In further study

### ➤ Employed soft switching

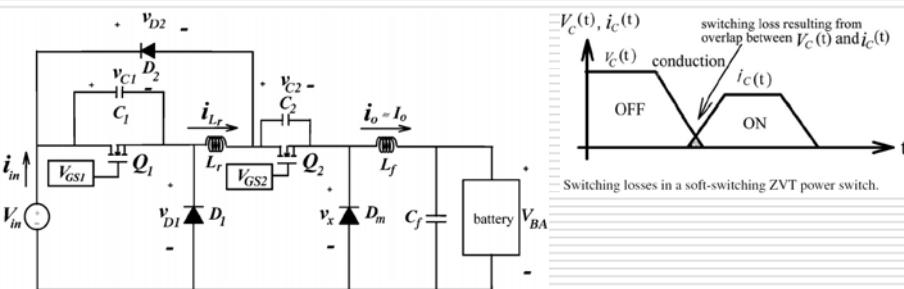

2011/01/25

48



Thanks for you attention !

